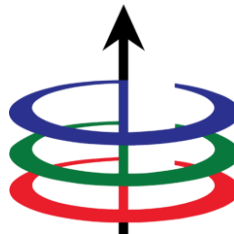


University of the Philippines Diliman
College of Engineering
Electrical and Electronics Engineering Institute

Capacitors and Inductors

1st Semester, A.Y. 2026–2027



Student Outcomes

- Recall the properties and behavior of capacitors and inductors, and their voltage-current relationship
- Calculate the voltage, current, power, and energy of capacitors and inductors
- Simplify a network of capacitors and inductors

Lecture Outline

- Fundamental Characteristics and Operation of Capacitors
- Fundamental Characteristics and Operation of Inductors
- Important characteristics of basic elements

Capacitors

A **capacitor** consists of **two conducting plates** separated by an **insulator or dielectric**. It stores energy in its electric field.

Common applications:

- Tuning circuits of radio receivers
- Dynamic memory elements




Figure. Different capacitors. Image reproduced from [Wikimedia](#).

Capacitance

ratio of the **charge on one plate** of a capacitor to the **voltage between the two plates**, measured in farads (F)

$$C = \frac{q}{v}$$

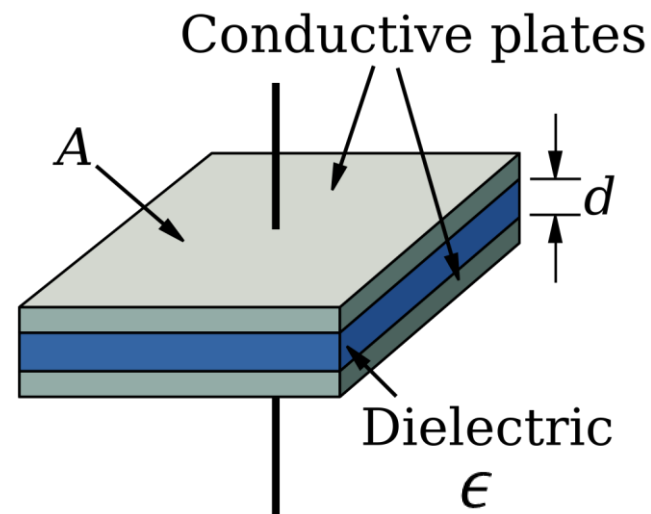capacitance
depends on its
**physical
dimensions!**



$$C = \epsilon \frac{A}{d}$$

Figure. Parallel-plate capacitor. Image reproduced from [Wikimedia](#).

Current-voltage relationship of capacitors

What is the current-voltage relationship in terms of voltage?

capacitance


$$C = \frac{q}{v}$$

current

$$i = \frac{dq}{dt}$$

current-voltage relationship

$$i = C \frac{dv}{dt}$$

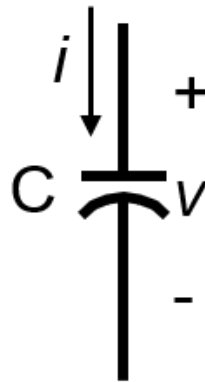

Power and energy of capacitors

- The power **delivered** to the capacitor is defined by the **voltage-current** product:

$$p(t) = v_C(t)i_C(t) = v_C(t) \left(C \frac{dv_C(t)}{dt} \right)$$

- The energy **stored** in the capacitor is given by:

$$\int_{t_0}^t p(t) dt = \int_{t_0}^t v_C(t) \left(C \frac{dv_C(t)}{dt} \right) dt = C \int_{t_0}^t v_C(t) dv_C(t)$$


$$w_C(t) - w_C(t_0) = \frac{1}{2} C ([v_C(t)]^2 - [v_C(t_0)]^2)$$

Remarks on the properties of capacitor

- When the **voltage across a capacitor is not changing with time**, the **current through the capacitor is zero**.
- The voltage on the capacitor **must be continuous**.
- The **ideal capacitor does not dissipate energy**.
- A real, non-ideal capacitor has a **parallel-mode leakage resistance**.

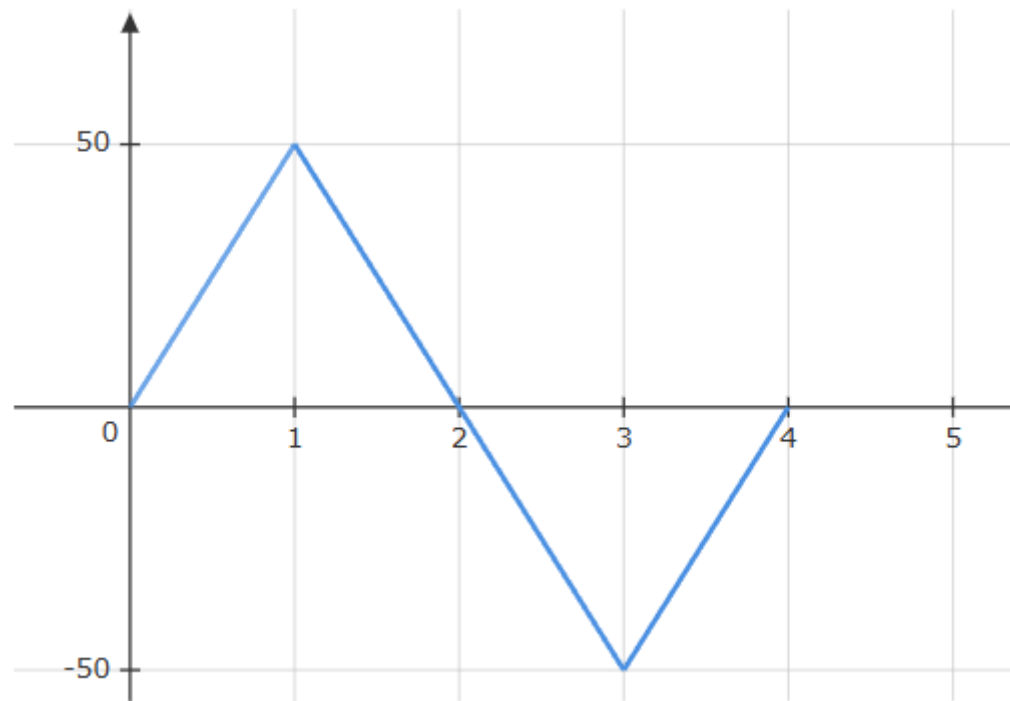
Example: Voltage-Current Curve

Determine the current through a $200\ \mu\text{F}$ capacitor whose voltage is shown in the graph below.



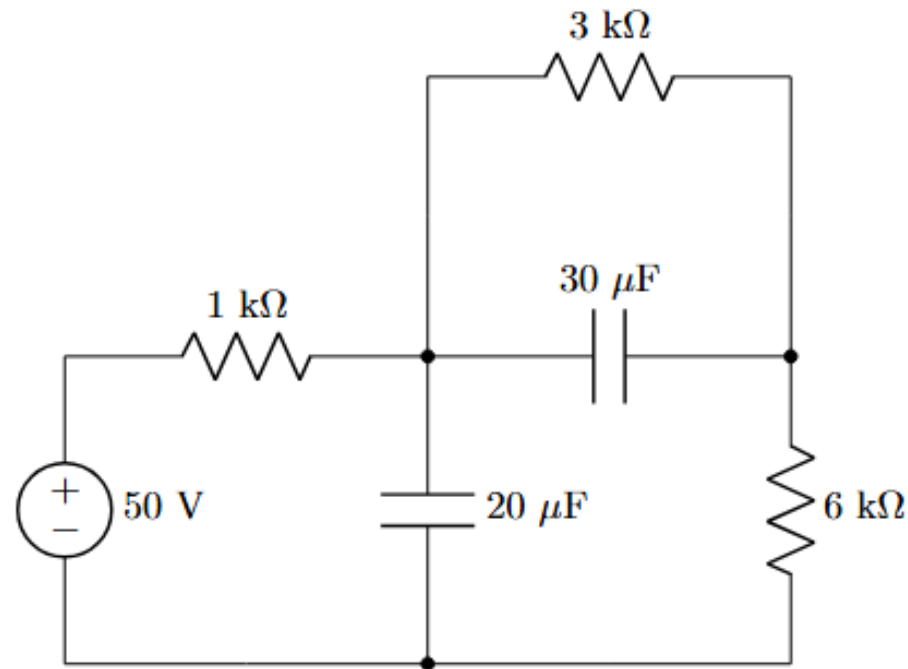Example: Capacitors in DC Circuits

Obtain the energy stored in each capacitor shown in the figure under DC conditions.



Parallel Capacitors

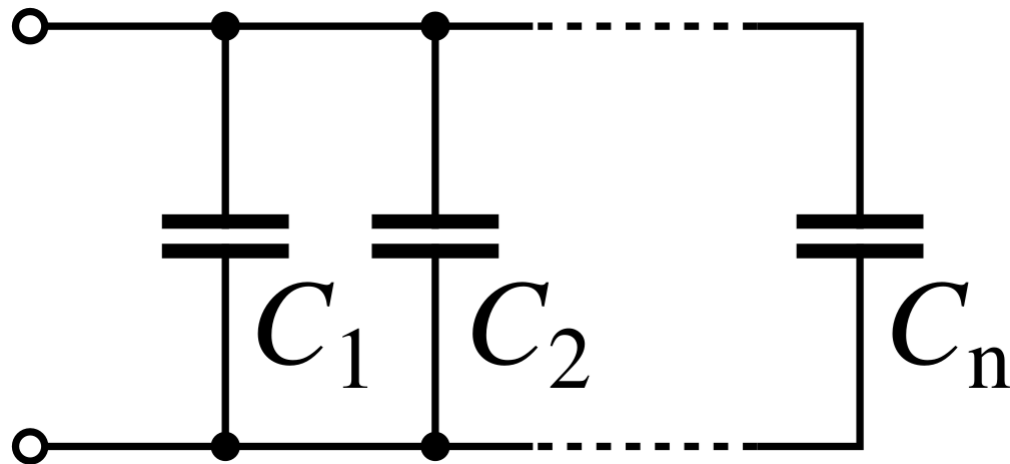


Figure. Parallel capacitors. Image reproduced from [Wikimedia](#).

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \cdots + C_N \frac{dv}{dt}$$

$$i = \frac{dv}{dt} \sum_{i=1}^N C_i$$

$$C_{eq} = \sum_{i=1}^N C_i$$

Series Capacitors

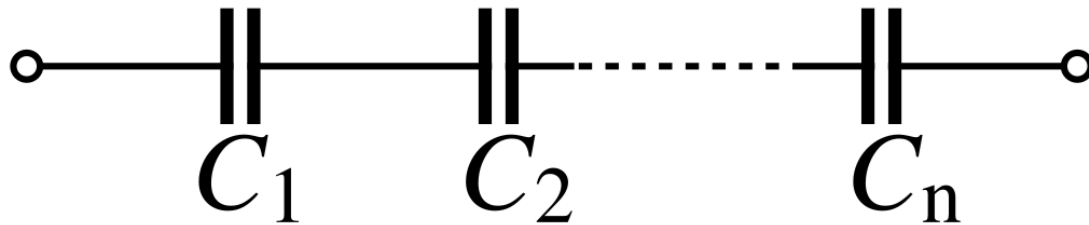


Figure. Series capacitors. Image reproduced from [Wikimedia](#).

$$v = v_{C1} + v_{C2} + v_{C3} + \cdots + v_{CN}$$


$$v = \frac{1}{C1} \int_{t_0}^t i(\tau) d\tau + \cdots + \frac{1}{CN} \int_{t_0}^t i(\tau) d\tau$$

$$i = \sum_{i=1}^N \frac{1}{C_i} \left(\int_{t_0}^t i(\tau) d\tau \right)$$

$$C_{eq} = \left(\sum_{i=1}^N \frac{1}{C_i} \right)^{-1}$$

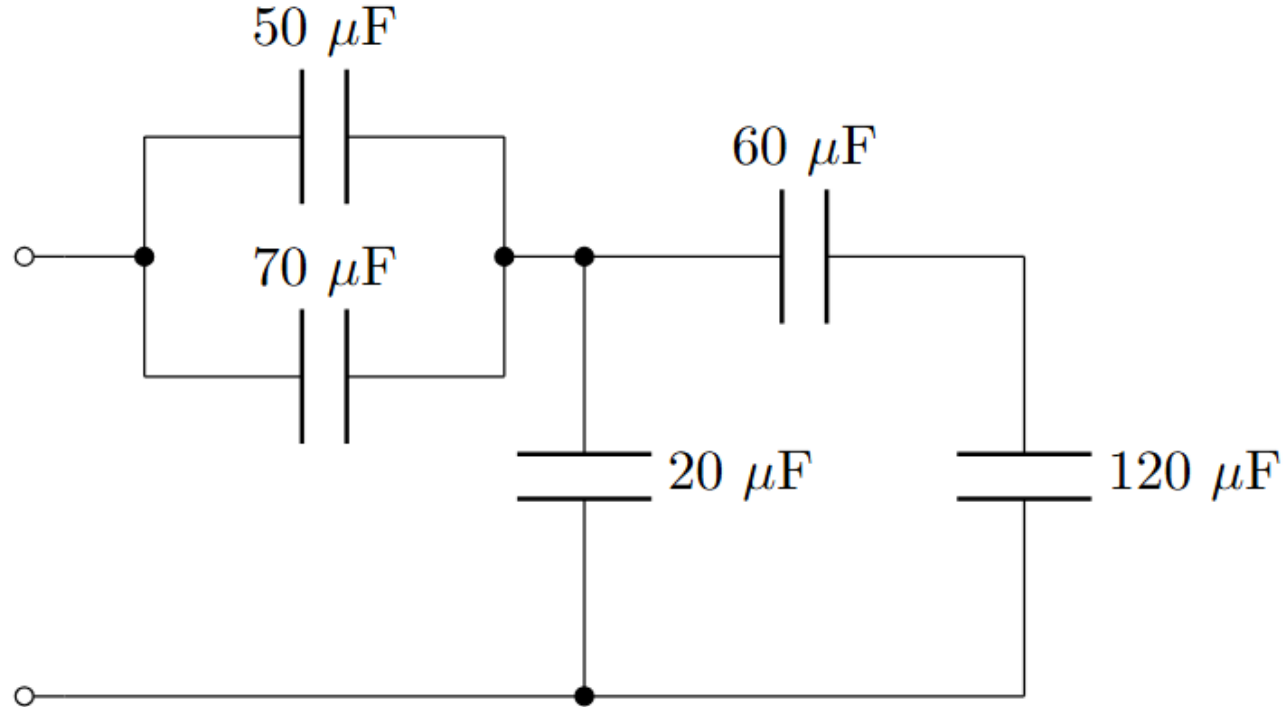Example: Equivalent Capacitance

Find the equivalent capacitance seen at the terminals of the circuit shown.



Inductors

An **inductor** consists of a **coil of conducting wire**. It stores energy in its magnetic field.

Common applications:

- Electronic and power systems
- Communication systems

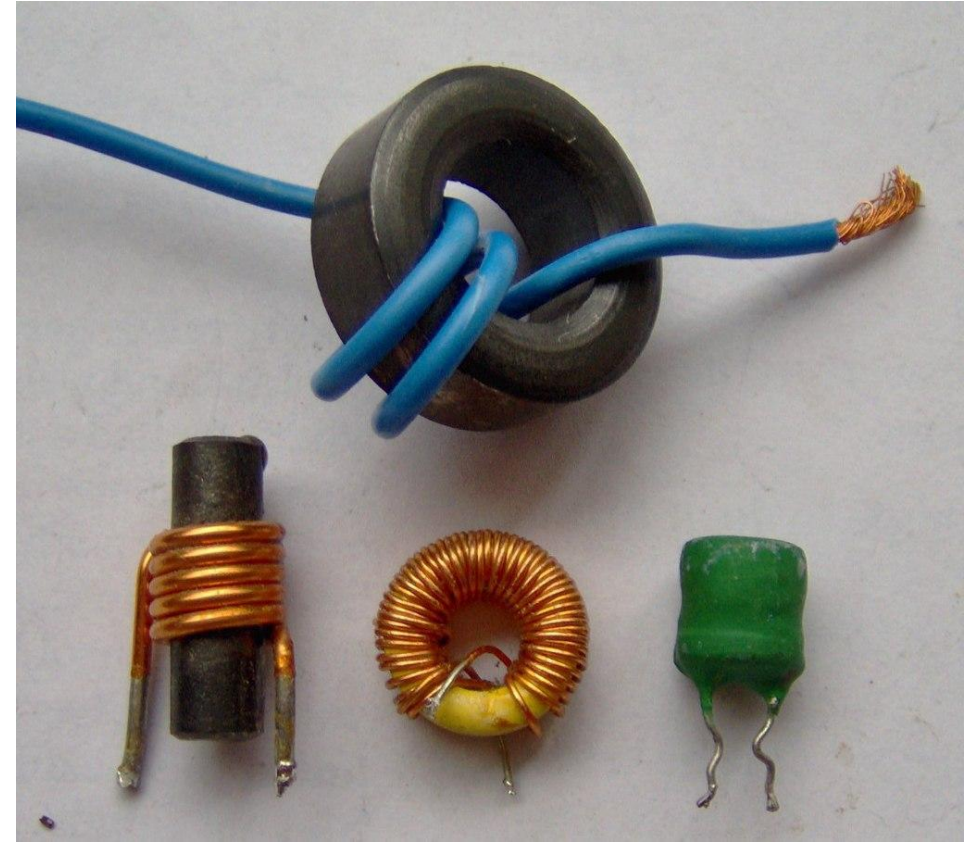


Figure. Different inductors. Image reproduced from [Wikimedia](#).

Inductance

ratio of the **magnetic flux linkage** generated by a given **current flowing through the inductor**, measured in henrys (H)

$$L = \frac{\Phi_B}{i}$$

inductance depends on its **physical dimensions!**

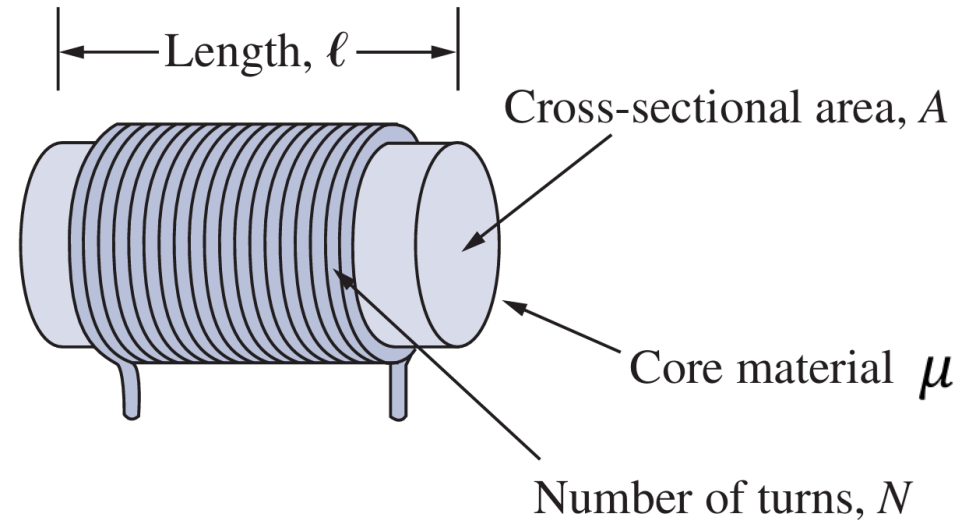


Figure. Typical form of an inductor. Image reproduced from [electrical-engineering-portal](#).

$$L = \frac{N^2 \mu A}{\ell}$$

Current-voltage relationship of inductors

Faraday's law of induction

$$v = \frac{d\phi_B}{dt}$$

inductance


$$L = \frac{\phi_B}{i}$$

What is the current-voltage relationship in terms of current?

modified to accommodate passive sign convention

current-voltage relationship

$$v = L \frac{di}{dt}$$

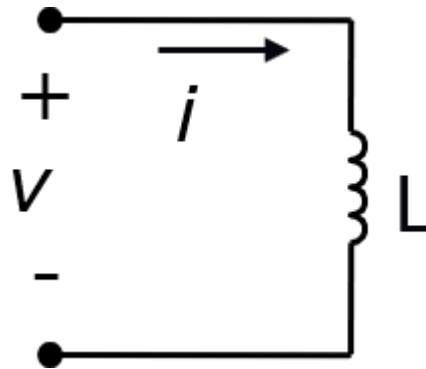

Power and energy of inductors

- The power **delivered** to the inductor is defined by the **voltage-current** product:

$$p(t) = v_L(t)i_L(t) = \left(L \frac{di_L(t)}{dt} \right) i_L(t)$$

- The energy **stored** in the inductor is given by:

$$\int_{t_0}^t p(t) dt = \int_{t_0}^t \left(L \frac{di_L(t)}{dt} \right) i_L(t) dt = L \int_{t_0}^t i_L(t) di_L(t)$$

$$w_L(t) - w_L(t_0) = \frac{1}{2} L ([i_L(t)]^2 - [i_L(t_0)]^2)$$

Remarks on the properties of inductor


- When the **voltage across an inductor is zero**, then **current through the inductor is constant**.
- The current through an inductor **must be continuous**.
- The **ideal inductor does not dissipate energy**.
- A real, non-ideal inductor has a **winding resistance**.

Example: Voltage Equation

The terminal voltage of a 2 H inductor is $v_L(t) = 10(1 - t)$ V. Find the current flowing through it at $t=4$ s and the energy stored in it at $t=4$ s. Assume $i_L(0) = 2$ A.

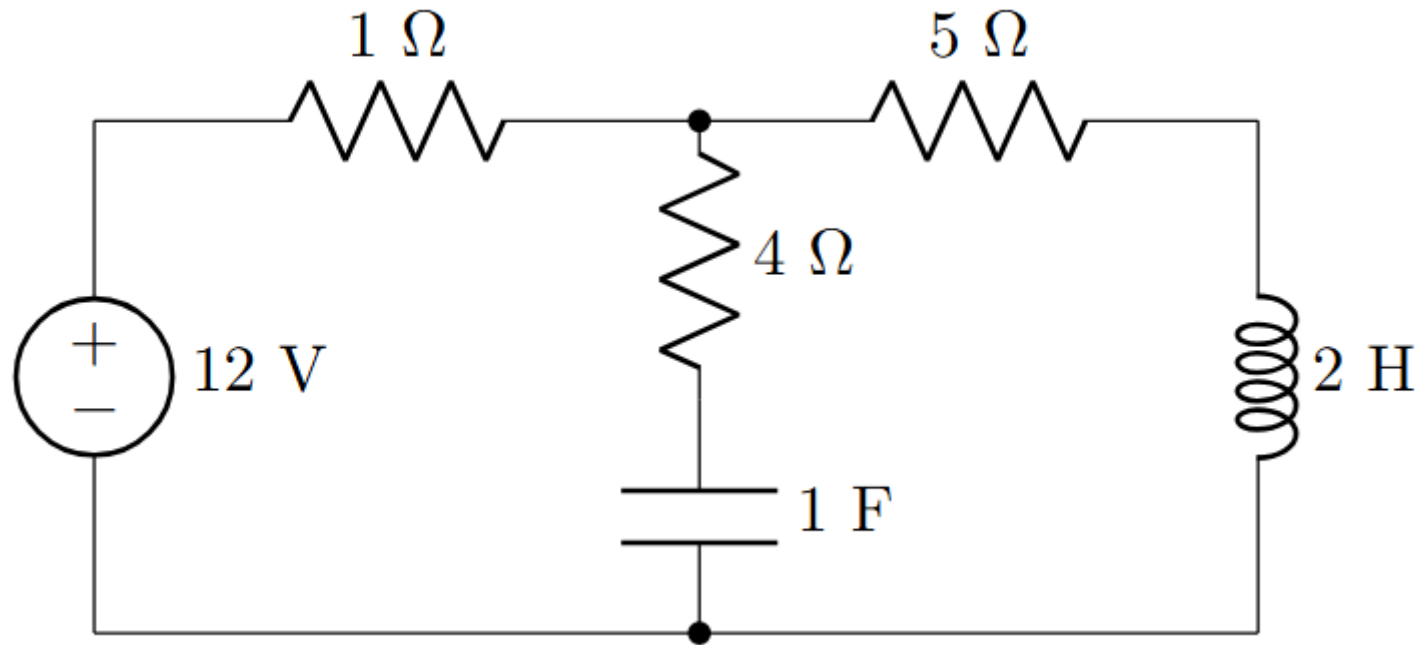Example: Inductors (and Capacitors) in DC Circuits

Obtain the energy stored in the capacitor and inductor shown in the figure under DC conditions.



Parallel Inductors

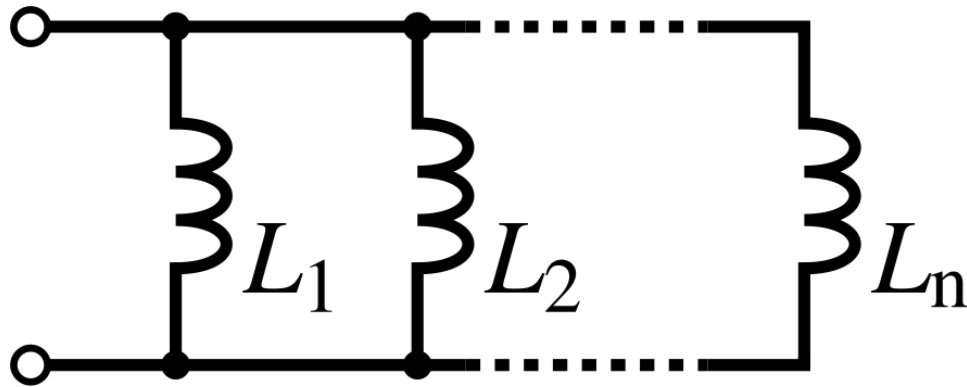


Figure. Parallel inductors. Image reproduced from [Wikimedia](#).

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = \frac{1}{L_1} \int_{t_0}^t v(\tau) d\tau + \cdots + \frac{1}{L_N} \int_{t_0}^t v(\tau) d\tau$$

$$i = \sum_{i=1}^N \frac{1}{L_i} \left(\int_{t_0}^t v(\tau) d\tau \right)$$

$$L_{eq} = \left(\sum_{i=1}^N \frac{1}{L_i} \right)^{-1}$$

Series Inductors

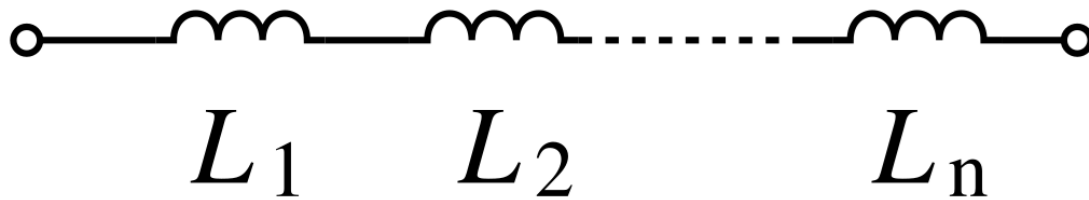


Figure. Series inductors. Image reproduced from [Wikimedia](#).

$$v = v_{L1} + v_{L2} + v_{L3} + \cdots + v_{LN}$$


$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \cdots + L_N \frac{di}{dt}$$

$$v = \frac{di}{dt} \sum_{i=1}^N L_i$$

$$L_{eq} = \sum_{i=1}^N L_i$$

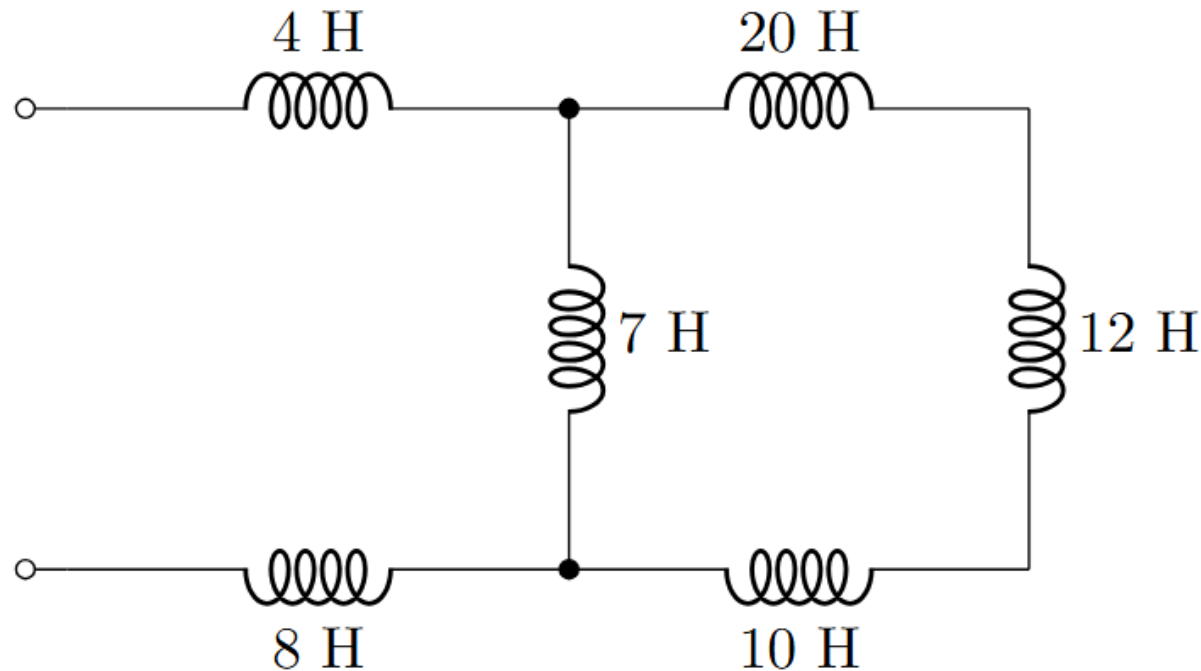Example: Equivalent Inductance

- Find the equivalent inductance seen at the terminals of the circuit shown.



Important characteristics of the basic elements

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v - i :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
i - v :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Summary

- Capacitors resist changes in voltage and store energy in their electric field.
- Inductors resist changes in current and store energy in their magnetic field.
- Under steady-state DC conditions, a capacitor acts as an open circuit while an inductor acts as a short circuit.
- However, an unenergized capacitor acts as a short circuit while an unenergized inductor acts as an open circuit.